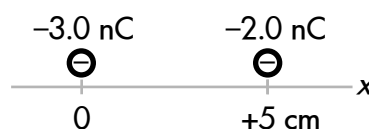


Closed book. Clearly circle your choice. No work needs to be shown for multiple-choice questions. No partial credit is given for multiple-choice questions.

1. [3.0 points.] Two point charges lie along the x -axis. A -3.0 nC charge is held at the origin, and a -2.0 nC charge is at $x = +5$ cm. In order to decrease their electric potential energy (make it a smaller positive number), the -2.0 nC charge should be moved to the:
- (A) left.
 - (B) right.
 - (C) (Both of the above choices.)
 - (D) (Neither of the above choices; this change in electric potential energy is impossible.)
 - (E) (Not enough information is given.)



For questions (2)-(3), a 0.024 nF capacitor is made from two foil sheets with a plastic spacer between them. The foil sheets are connected to a 9.0 V battery.

2. [3.0 points.] The charge stored in this capacitor is:
- (A) 3.8×10^{11} C.
 - (B) 2.2×10^{-10} C.
 - (C) 2.7×10^{-12} C.
 - (D) 9.8×10^{-10} C.
3. [3.0 points.] If the foil sheets of this capacitor are instead connected to a 15.0 V battery, its _____ would increase.
- (A) capacitance.
 - (B) charge.
 - (C) (Both of the above choices.)
 - (D) (Neither of the above choices.)
 - (E) (Not enough information is given.)

4. [3.0 points.] Electric potential is measured in units of:
- (A) A (amperes).
 - (B) C (coulombs).
 - (C) F (farads).
 - (D) J (joules).
 - (E) N/C (newtons per coulomb).
 - (F) Ω (ohms).
 - (G) V (volts).
 - (H) W (watts).

5. [3.0 points.] The unit of J (joules) is a measure of:
- (A) electric field.
 - (B) electric potential.
 - (C) electric potential energy.
 - (D) power.
 - (E) charge.
 - (F) current.
 - (G) resistance.
 - (H) capacitance.

Questions (5)-(10) are continued on the back of this page.

Equations and constants:


$$|e| = 1.602 \times 10^{-19} \text{ C}; k = 8.99 \times 10^9 \frac{\text{N} \cdot \text{m}^2}{\text{C}^2}; EPE = k \frac{q_1 q_2}{r}; \Delta EPE = q(\Delta V); V = k \frac{Q}{r}.$$

$$C = \frac{Q}{\Delta V}; C = \frac{A}{4\pi k d}; \Delta V = -Ed; EPE = \frac{1}{2} Q(\Delta V).$$

Closed book. Clearly circle your choice. No work needs to be shown for multiple-choice questions. No partial credit is given for multiple-choice questions.

This quiz continues from questions (1)-(5) on the other side of this page.

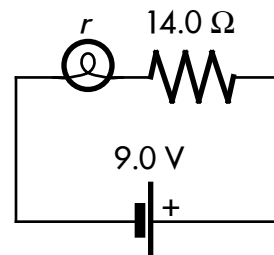For questions (6)-(8), a light bulb (of unknown resistance r) and a 14.0Ω resistor are connected to an ideal 9.0 V emf source. The current flowing through the light bulb is 0.59 A .




6. [3.0 points.] The current flowing through the resistor is _____ 0.59 A .
 - (A) less than.
 - (B) equal to.
 - (C) greater than.
 - (D) (Not enough information is given.)

7. [3.0 points.] The current flowing through the emf is _____ 0.59 A .
 - (A) less than.
 - (B) equal to.
 - (C) greater than.
 - (D) (Not enough information is given.)

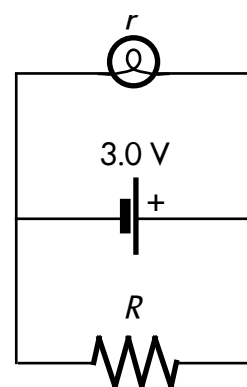8. [3.0 points.] The equivalent resistance of this circuit is _____ 14.0Ω .
 - (A) less than.
 - (B) equal to.
 - (C) greater than.
 - (D) (Not enough information is given.)

For questions (9)-(10), a light bulb (of unknown resistance r) and a resistor (of unknown resistance R) are connected to an ideal 3.0 V emf source. The current flowing through the light bulb is 0.8 A , and the current flowing through the resistor is 1.4 A .



9. [3.0 points.] The current flowing through the emf source is:
 - (A) 0.51 A .
 - (B) 1.8 A .
 - (C) 2.2 A .
 - (D) 5.2 A .

10. [3.0 points.] The equivalent resistance of this circuit is:
 - (A) 0.51Ω .
 - (B) 1.4Ω .
 - (C) 2.1Ω .
 - (D) 3.8Ω .

Equations and constants:

$$I = \frac{\Delta q}{\Delta t}; \quad I = \frac{\Delta V}{R}; \quad P = I(\Delta V); \quad \sum I_{in} = \sum I_{out}; \quad \sum_{loop} \Delta V_{rises} = \sum_{loop} \Delta V_{drops}; \quad R_{eq} = \sum R_i; \quad \frac{1}{R_{eq}} = \sum \frac{1}{R_i}.$$